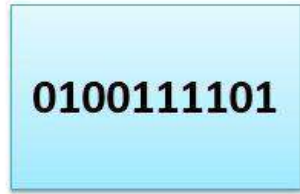


Analog
Signal

Vs




Digital
Signal

Subject -ADIC

ANALOG AND DIGITAL INTEGRATED CIRCUIT

(SEM-4)

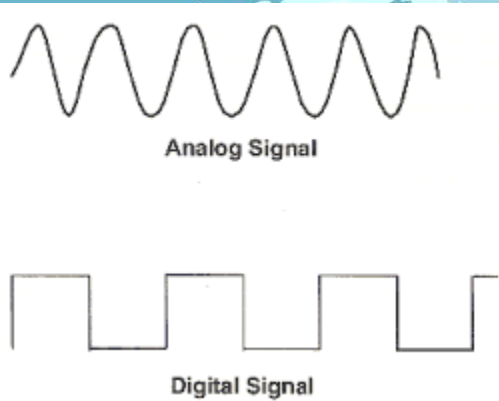

ANALOG???



- ❖ Analog signal is a continuous signal which represents physical measurements.
- ❖ Denoted by sine waves.
- ❖ Uses continuous range of values to represent information.
- ❖ Human voice in air, analog electronic devices are the examples of the analog signal.
- ❖ Subjected to deterioration by noise during transmission and write/read cycle.
- ❖ Low cost and portable.
- ❖ Analog instrument draws large power.
- ❖ Can be used in analog devices only, Best suited for audio and video transmission.

DIGITAL???



- ❖ Digital signals are discrete time signals generated by digital modulation.
- ❖ Denoted by square waves.
- ❖ Uses discrete or discontinuous values to represent information.
- ❖ Computers, CDs, DVDs, and other digital electronic devices.
- ❖ Can be noise-immune without deterioration during transmission and write/read cycle.
- ❖ Cost is high and not easily portable.
- ❖ Digital instrument draws only negligible power.
- ❖ Best suited for Computing and digital electronics.



INTEGRATED CIRCUIT ???




INTEGRATED CIRCUIT

Integrated circuit (IC), also called microelectronic circuit, microchip, or chip, an assembly of electronic components, fabricated as a single unit, in which miniaturized active devices (e.g., transistor and diodes) and passive devices (e.g., capacitors and resistors) and their interconnections are built up on a thin substrate of Semiconductor material (typically Silicon). The resulting circuit is thus a small “chip,” which may be as small as a few square centimeters or only a few square millimeters. The individual circuit components are generally microscopic in size.


Op-amp Transfer Characteristics:

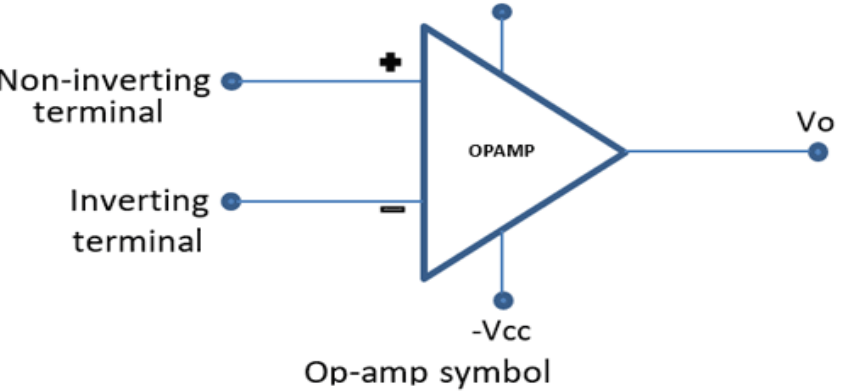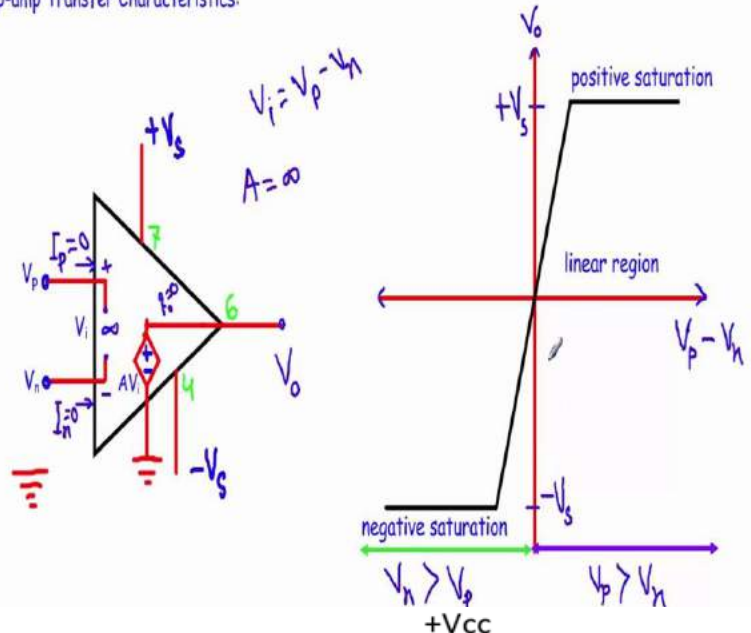

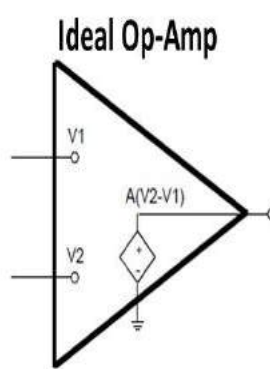
Op-Amp Ideal, Equivalent Circuit, Characteristics and Features



Op-Amp Equivalent Circuit

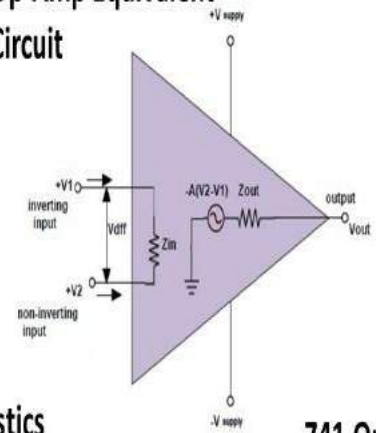

Op-Amp Symbol

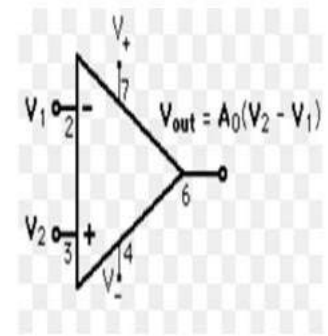


Op-Amp Characteristics

Parameter	Ideal Op-Amp	Typical Op-Amp
G_{OL}	∞	$10^5 - 10^9$
Common Mode Gain	0	10^{-5}
Bandwidth	∞	1-20 MHz
Input Impedance	∞	$10^6 \Omega$ (bipolar) $10^9 - 10^{12} \Omega$ (FET)
Output Impedance	0	100-1000 Ω


741 Op-Amp Features

741 in 8-pin DIL (Dual In Line) pack

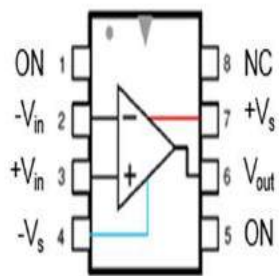

- $+V_2$: Non-inverting input
- $-V_1$: Inverting input
- $+V_s$: Positive source PS
- $-V_s$: Negative source PS
- V_{out} : Output voltage
- ON: Offset Null
- NC: Not Connected

BLOCK DIAGRAM OF OPERATIONAL AMPLIFIER

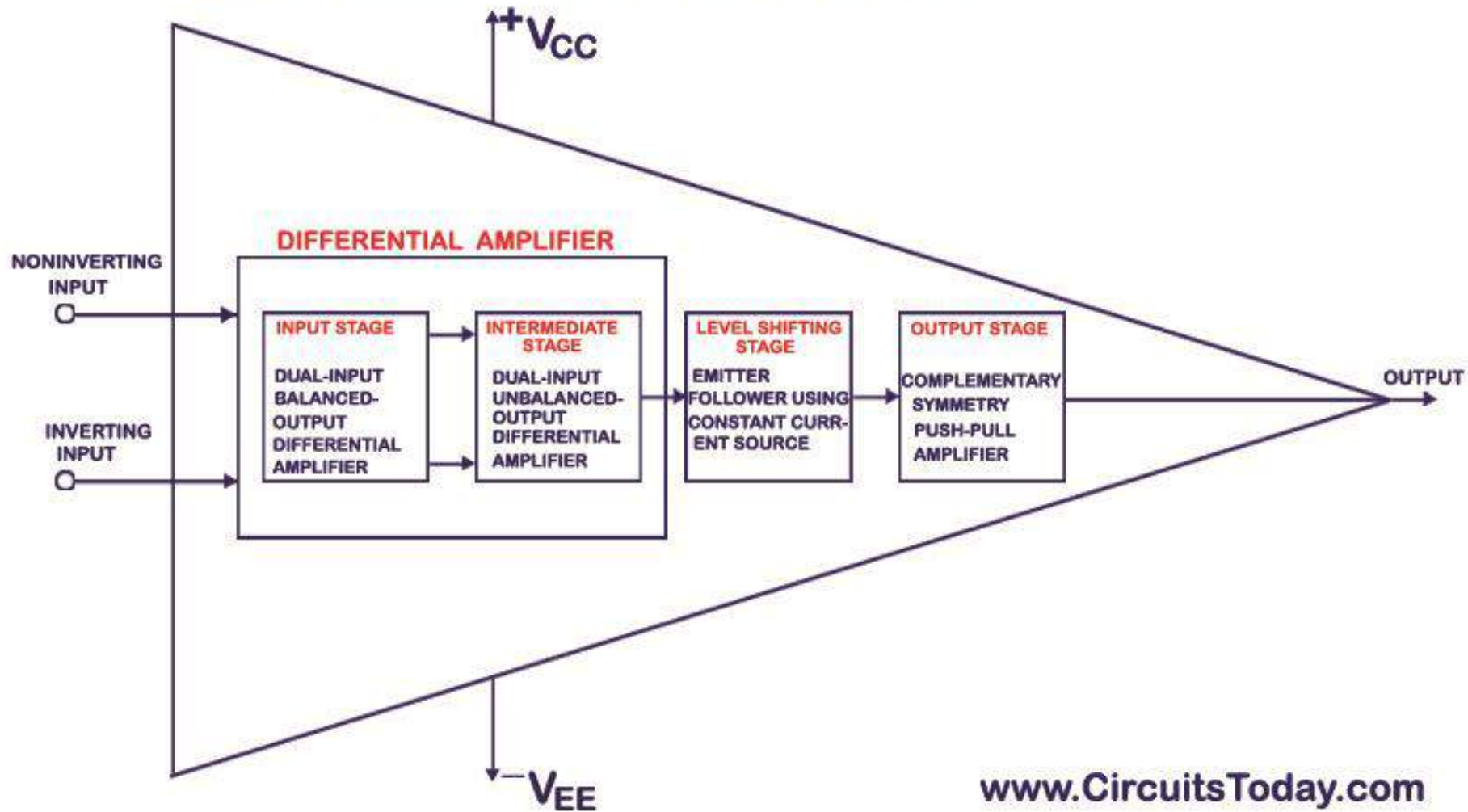

Frequency Response of Op-amp

- The voltage or current gain of an amplifier expressed in dB is $20 \log_{10} |A|$, where $A = V_{out}/V_{in}$.
- The frequency response of an op-amp has a low-pass characteristic (passing low-frequency signals, attenuating high-frequency signals).

